
Grundlagen der Rechnerarchitektur

Tim Luchterhand, Paul Nykiel (Abgabegruppe 117)

1. Februar 2019


1

 



 T_6 :T=0 \ A=11, L=0, C=1

Transition	Etagen- sensor	Fahrstuhl- panel		Zeit- Prüfer	Zustand		Folge- zustand	
T	E	EG	OG	Т	q₁	\mathbf{q}_0	d₁	d_0
To	d	0	0	d	0	0	0	0
\mathbf{T}_1	1	1	0	d	0	0	0	1
\mathbb{T}_2	1	d	d	d	0	1	0	1
Т3	0	d	d	d	0	1	0	0
T ₄	0	1	0	d	0	0	1	0
T_5	1	0	1	d	0	0	1	0
\mathbb{T}_6	d	d	d	0	1	0	1	0
${f T}_7$	d	d	d	1	1	0	0	0
Т8	0	0	1	d	0	0	1	1
Т9	0	d	d	d	1	1	1	1
T ₁₀	1	d	d	d	1	1	0	0

Ausgang		Timer						
a ₁	a ₀	n ₂	n ₁	n ₀	L	С		
0	0	d	d	d	d	d		
1	0	d	d	d	d	d		
1	0	d	d	d	d	d		
0	0	d	d	d	d	d		
1	1	1	1	0	1	0		
1	1	1	1	0	1	0		
1	1	d	d	d	0	1		
0	0	d	d	d	d	d		
0	1	d	d	d	d	d		
0	1	d	d	d	d	d		
0	0	d	d	d	d	d		

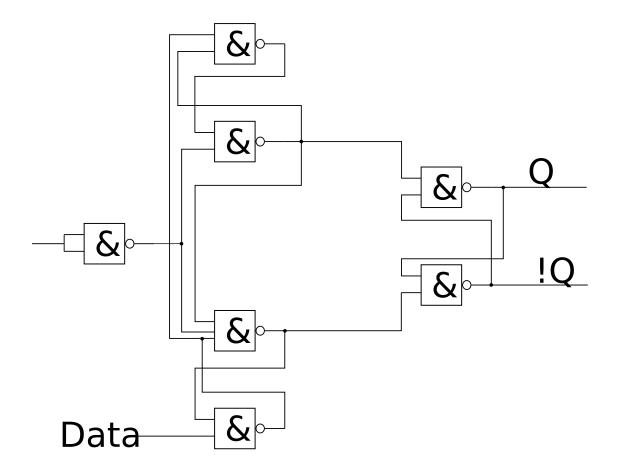

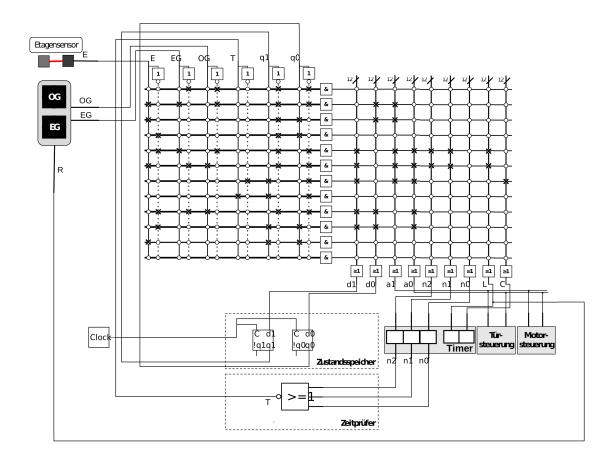

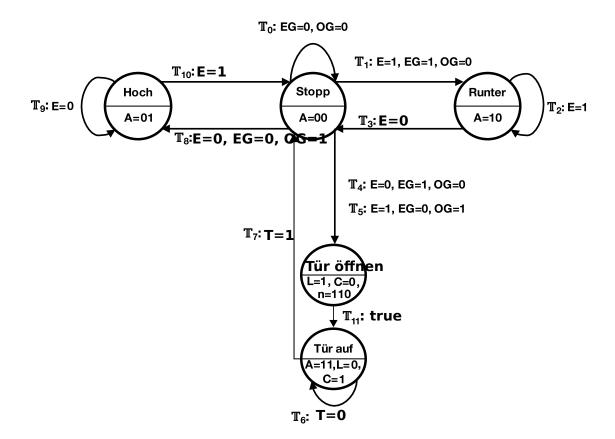

Transition	Etagen- sensor		stuhl- nel	Zeit- Prüfer	Zustand		Folge- zustand	
T	E	EG	OG	Т	q ₁	\mathbf{q}_0	d₁	d_0
To	d	0	0	d	0	0	0	0
\mathbf{T}_1	1	1	0	d	0	0	0	1
\mathbb{T}_2	1	d	d	d	0	1	0	1
Т3	0	d	d	d	0	1	0	0
\mathbb{T}_4	0	1	0	d	0	0	1	0
\mathbb{T}_5	1	0	1	d	0	0	1	0
\mathbb{T}_6	d	d	d	0	1	0	1	0
T ₇	d	d	d	1	1	0	0	0
Т8	0	0	1	d	0	0	1	1
Т9	0	d	d	d	1	1	1	1
T ₁₀	1	d	d	d	1	1	0	0

Ausgang		Timer						
a ₁	\mathbf{a}_0	n ₂	n ₁	n _o	L	С		
0	0	đ	а	d	d	d		
1	0	d	d	d	d	d		
1	0	d	d	d	d	d		
0	0	d	d	d	d	d		
1	1	1	1	0	1	0		
1	1	1	1	0	1	0		
1	1	d	d	d	0	1		
0	0	d	d	d	d	d		
0	1	d	d	d	d	d		
0	1	d	d	d	d	d		
0	0	d	d	d	d	d		